



# DCS Lab 5

## Finite State Machine

---

葉曜銘

# Purpose

- Learn how to design a finite state machine (FSM) using Verilog.

# Lab05

- Run the command below to get files for this lab.
  - `tar -xvf ~dcsTA01/Lab05.tar`


# Branch

- Some common branch instruction in RISC-V ISA:
  1. BEQ (Branch if Equal)
  2. BNE (Branch if Not Equal)
  3. BLT (Branch if Less Than)
  4. BGE (Branch if Greater or Equal)

Instruction	Branch taken	Branch not taken
BEQ A, B, dest	$A == B$	$A != B$
BNE A, B, dest	$A != B$	$A == B$
BLT A, B, dest	$A < B$	$A >= B$
BGE A, B, dest	$A >= B$	$A < B$

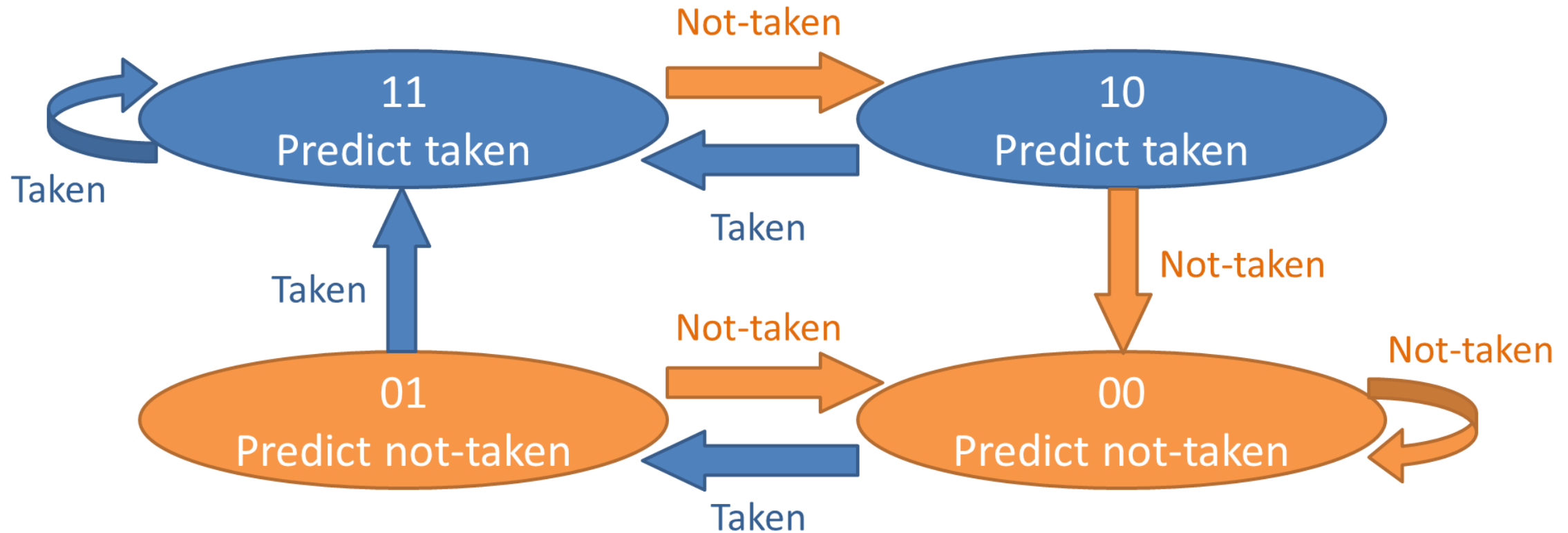
# Problem for This Lab: 2-bit Branch Predictor

- Predicting a branch is taken or not can speed up the execution.
- 2-bit branch predictor change its prediction if two misses occur.


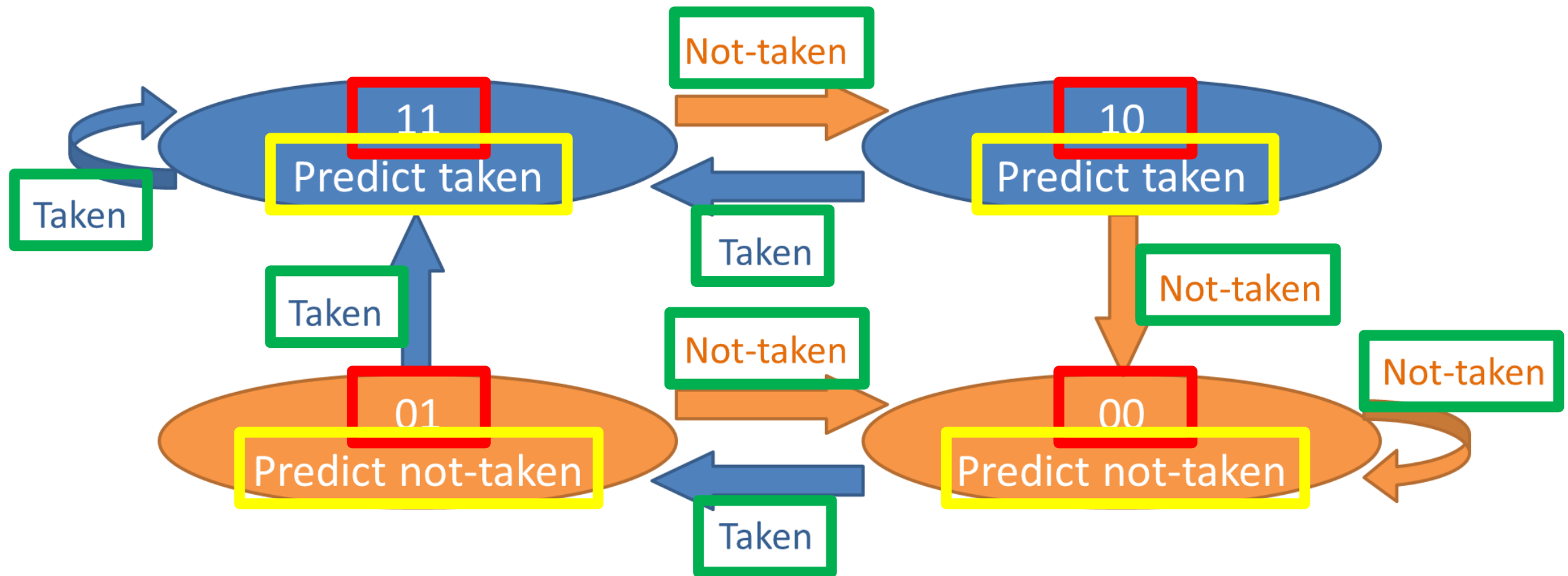
# 2-bit Branch Predictor as a FSM

- **State**, **output**, **condition** (generated from inputs and current state)




# FSM.sv

Input Signal	Bit Width	Definition
clk	1	Clock.
rst_n	1	Asynchronous active-low reset.
in_valid	1	High when input is valid.
op	2	Type of branch instruction. <b>(BEQ=00, BNE=01, BLT=10, BGE=11)</b>
A	4	The first variable for branch instruction.
B	4	The second variable for branch instruction.

Output Signal	Bit Width	Definition
pred_taken	1	High when the prediction is taken. <b>Should be reset when rst_n is low.</b>
state	2	Current state of your 2-bit predictor. <b>Should be reset when rst_n is low.</b>

## FSM.sv

Instruction	Branch taken	Branch not taken
BEQ A, B, dest	A == B	A != B
BNE A, B, dest	A != B	A == B
BLT A, B, dest	A < B	A >= B
BGE A, B, dest	A >= B	A < B

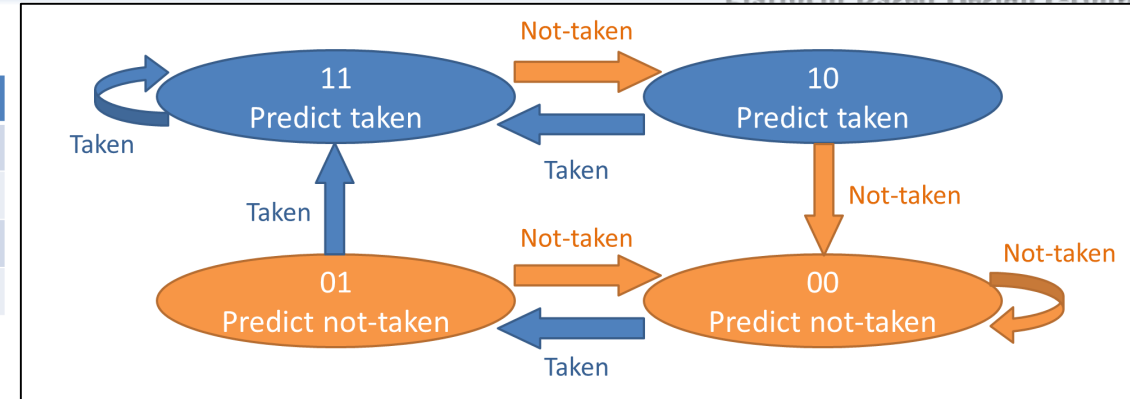

All outputs should be reset when rst\_n is low


BGE 13, 13

BNE 9, 14

BEQ 9, 3

BLT 2, 12

BEQ 2, 11

 

Outputs should change at the posedge of clk if in\_valid is high

Outputs should NOT change if in\_valid is low



# Reminder

- 1. You must follow the state diagram in p.5.**
2. State should be reset to 2'b00 when rst\_n is low. (And pred\_taken should be low at the same time.)
3. Outputs should change at posedge of clk if in\_valid is high. (unless the inputs don't change the state.)
4. Both pred\_taken and state should not change when in\_valid is low.

# Grading Policy

- Pass the RTL & Synthesis & Gate-level simulation: 100%
  - 合成結果: (不能有**Error**、**Timing report slack met**、不能有**Latch**)
  - Gate-level simulation不可以發生**timing violation**
- Demo 2 打7折

```
Warning! Timing violation
$hold( posedge RN:119954 FS, posedge SN:204217 FS, 0.229292 : 229292 FS );
File: /usr/cad/umc018/Verilog/umc18_neg.v, line = 9379
Scope: TESTBED.I_Seq.lose_reg
Time: 204217 FS
```

# Upload

- 請將Lab05/01\_RTL裡的**FSM.sv**依以下命名規則重新命名後上傳至E3
- 命名規則：**FSM\_dcsxxx.sv**，xxx為工作站帳號號碼
- **命名錯誤扣5分!!!**
- **Deadline:**
  - **Demo 1: 3/27 17:25**
  - **Demo 2: 3/27 23:59**