



Lab02

Counter

賴奕翔

Purpose

- Be familiar with Verilog syntax
 - Avoid multiple-driven
 - Separate sequential and combinational block
- Be familiar with circuit specification
 - Output data should be strictly **RESET !!!**
- Sequential circuit
- Counter

Sequential Circuit

- Different from combinational circuit, sequential circuit will synthesize registers which can store previous data.

```
always @(posedge clk or negedge rst_n) begin
    if(!rst_n)
        a <= 0;
    else
        a <= a + 1;
end
```

← Sequential circuit

```
assign a = a + 1;

always @(*) begin
    a = a + 1;
end

always @(*) begin
    if(a > b) a = b;
    else a = a;
end
```


← Combinational circuit

Waveform Difference

- Combinational Circuit

```
always@(*)begin
    if(in_valid) out_data = in_data;
    else out_data = 0;
end

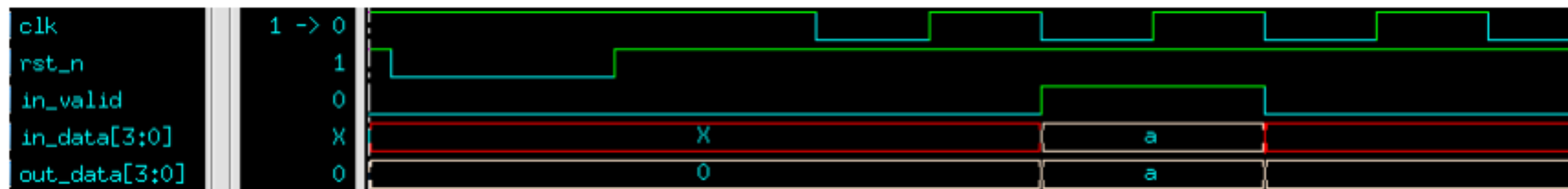
assign out_data = (in_valid) ? in_data : 0;
```



Waveform Difference

- Sequential Circuit

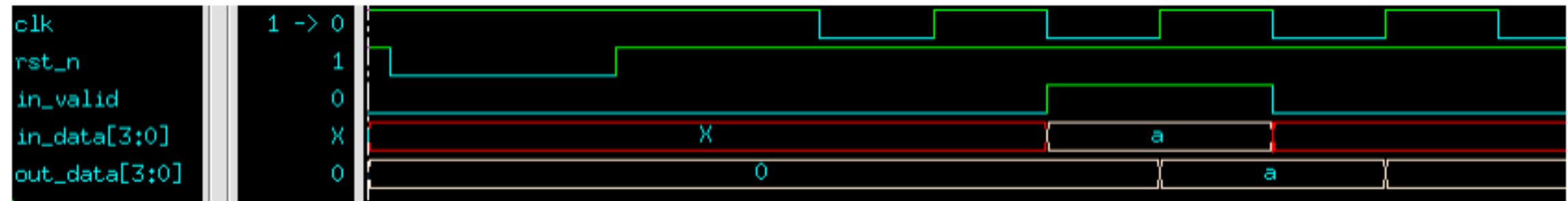
```
always@(posedge clk or negedge rst_n)begin
    if(!rst_n)
        out_data <= 0;
    else begin
        if(in_valid) out_data <= in_data;
        else out_data <= 0;
    end
end
end
```



Counter

- At the beginning, the pattern will send rst_n, you should reset out_num to 0
 - Reset when rst_n is low
- When the “in_valid” is high, the pattern will provide a number: in_num for counting
 - “in_valid” will be high for one cycle
 - The range of in_num is 1~31
- After receiving in_num, you should increment out_num from 0 to in_num over the following cycles
 - Once counting is finished, you should hold out_num (out_num = in_num) until the next pattern
- The next counting pattern will arrive in 2~6 cycles

Reference Block Diagram

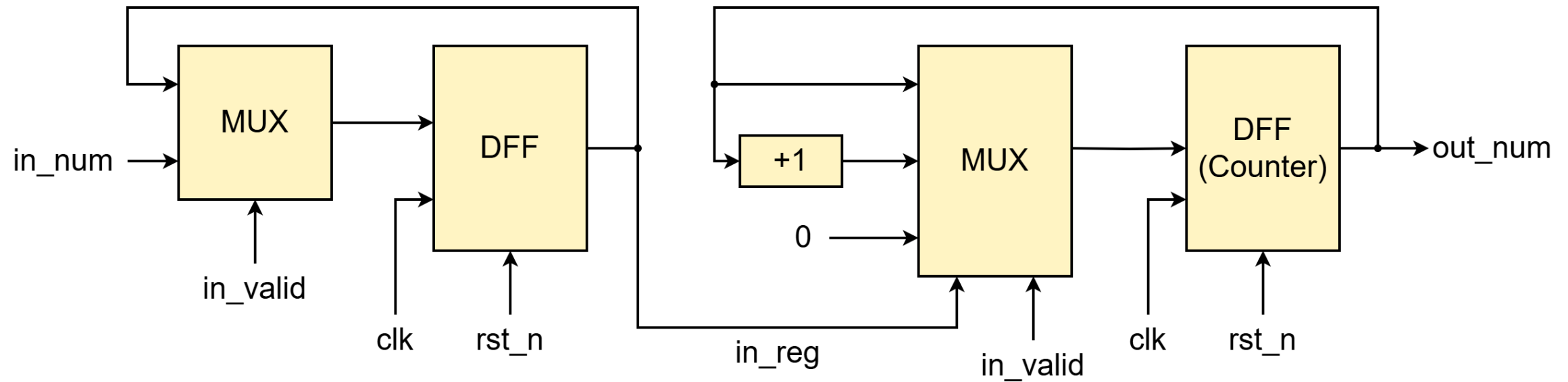


Specification

- Counter.sv


Input Signal	Bit Width	Definition
clk	1	Clock
rst_n	1	Asynchronous active-low reset
in_valid	1	High when input signal is ready
in_num	5	The number of cycles to count

Output Signal	Bit Width	Definition
out_num	5	Count from 0 to in_num after input, then hold out_num until next pattern arrives

Output and Waveform

 

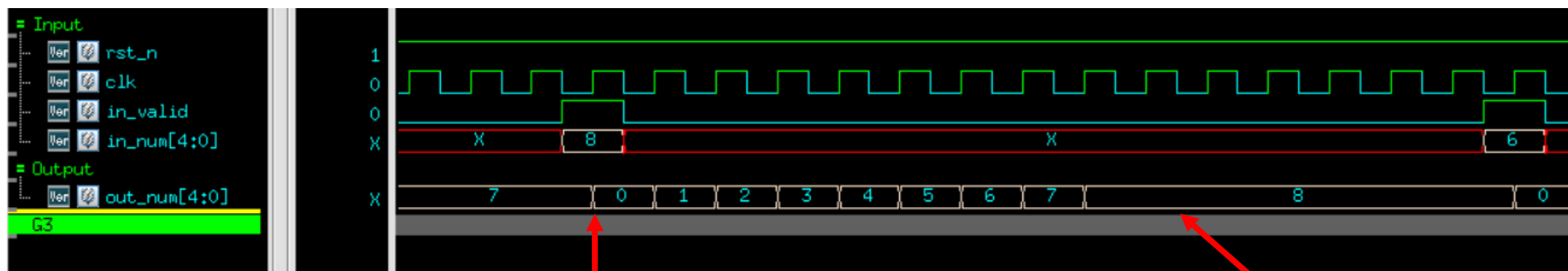out_num should be reset to zero when rst_n is low



start counting after input is received

hold out_num until next pattern

Separate sequential and combinational block

```
always_ff @(posedge clk, negedge rst_n) begin
    if(!rst_n) Q <= 0;
    else Q <= Q_next;
end
assign Q_next = A + B;
```

Good design

```
always_ff @(posedge clk, negedge rst_n) begin
    if(!rst_n) Q <= 0;
    else Q <= A + B;
end
```

Bad design

Directory


- 00_TESTBED
 - TESTBED.sv
 - PATTERN.sv
- 01_RTL
 - 01_run
 - 09_clean_up
 - Counter.sv
- 02_SYN
 - 01_run_dc
 - 09_clean_up
- 03_GATE
 - 01_run
 - 09_clean_up

Command

- `tar -xvf ~dcsTA01/Lab02.tar`
- `cd Lab02/01_RTL/`

RTL Simulation

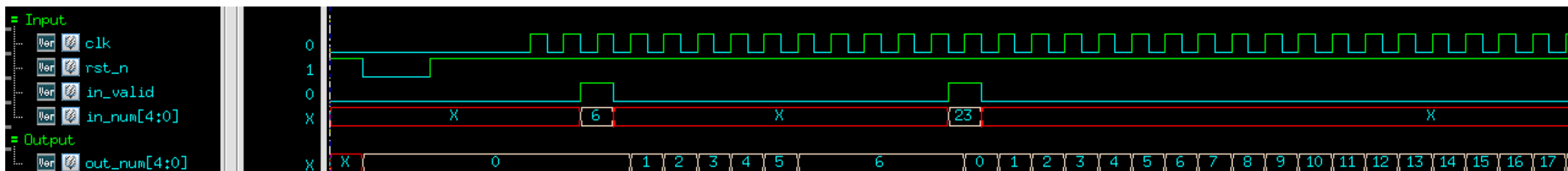- cd Lab02/01_RTL/
- ./01_run (電路模擬)
- ./09_clean_up (清除波型檔)
- nWave & (看波型)
 - 範例波型



Synthesis

- `cd ../02_SYN/`
- `./01_run_dc` (電路合成)
- `./09_clean_up` (清除合成結果)
 - 合成結果: (不能有Error、要有Area report、Timing report slack met、不能有Latch)

```
Number of ports: 13
Number of nets: 52
Number of cells: 44
Number of combinational cells: 34
Number of sequential cells: 10
Number of macros/black boxes: 0
Number of buf/inv: 8
Number of references: 15

Combinational area: 31.298400
Buf/Inv area: 3.628800
Noncombinational area: 45.359998
Macro/Black Box area: 0.000000
Net Interconnect area: 0.000000

Total cell area: 76.658397
Total area: 76.658397
```

Synthesis

- 合成的timing report中的slack必須 ≥ 0 (MET)
- 如果出現timing violation \rightarrow Demo Fail ! (slack < 0)

Point	Incr	Path
clock clk (rise edge)	0.00	0.00
clock network delay (ideal)	0.00	0.00
input external delay	5.00	5.00 r
in_valid (in)	0.00	5.00 r
U41/Y (INV_X0P5B_A9TR)	0.06	5.06 f
U42/Y (NAND2_X0P5A_A9TR)	0.10	5.16 r
U56/Y (NAND2_X0P5A_A9TR)	0.09	5.24 f
U61/Y (NOR2_X0P5A_A9TR)	0.10	5.35 r
U63/Y (OAI21_X0P5M_A9TR)	0.05	5.40 f
U64/Y (OAI31_X0P5M_A9TR)	0.07	5.47 r
out_num_reg_2_/D (DFFRPQ_X1M_A9TR)	0.00	5.47 r
data arrival time		5.47
clock clk (rise edge)	10.00	10.00
clock network delay (ideal)	0.00	10.00
out_num_reg_2_/CK (DFFRPQ_X1M_A9TR)	0.00	10.00 r
library setup time	-0.04	9.96
data required time		9.96
data required time		9.96
data arrival time		-5.47
slack (MET)		4.49

Synthesis


- 記得檢查是否合成出Latch和error
 - 可以在syn.log用ctrl+F尋找關鍵字Latch、error
- 如果出現Latch、error → Demo Fail

Register Name	Type	Width	Bus	MB	AR	AS	SR	SS	ST
in_num2_reg	Latch	1	N	N	N	N	-	-	-



Gate-Level Simulation

 - `cd ../03_GATE/`
- `./01_run` (電路模擬)
- `./09_clean_up` (清除波型檔)
- nWave & (看波型)
 - 範例波形



Grading Policy

- Pass the RTL & Synthesis & Gate-level simulation: 100%
 - 合成結果: (不能有Error、Timing report slack met、不能有Latch)
- Demo2 打7折

Upload

- 請將Lab02/01_RTL裡的Counter.sv依以下命名規則重新命名後上傳至E3
- 命名規則：Counter_dcsxxx.sv，xxx為工作站帳號號碼
- 命名錯誤扣5分!!!
- **Deadline:**
 - Demo 1: 3/6 17:25
 - Demo 2: 3/6 23:59